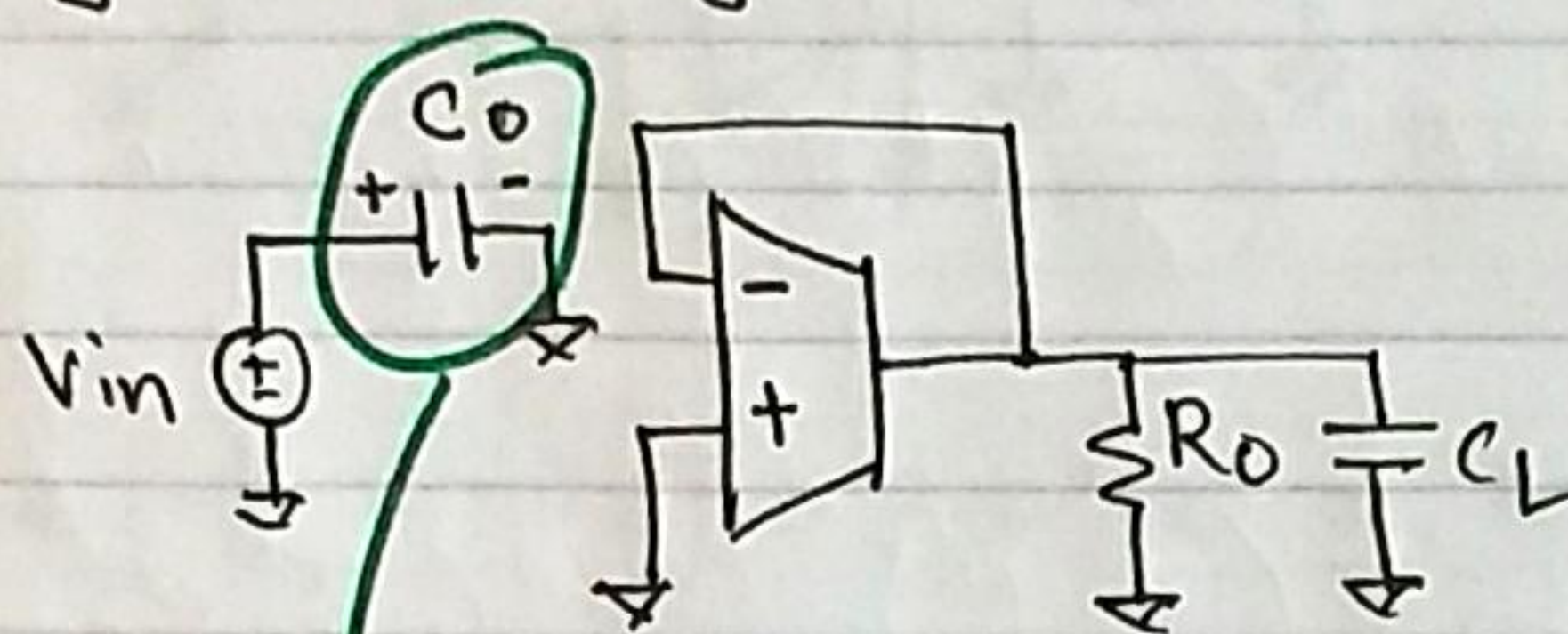



Settling behavior of the SW circuit

During sampling phase:




This is charged to V_{in}

During amplifier amplification phase

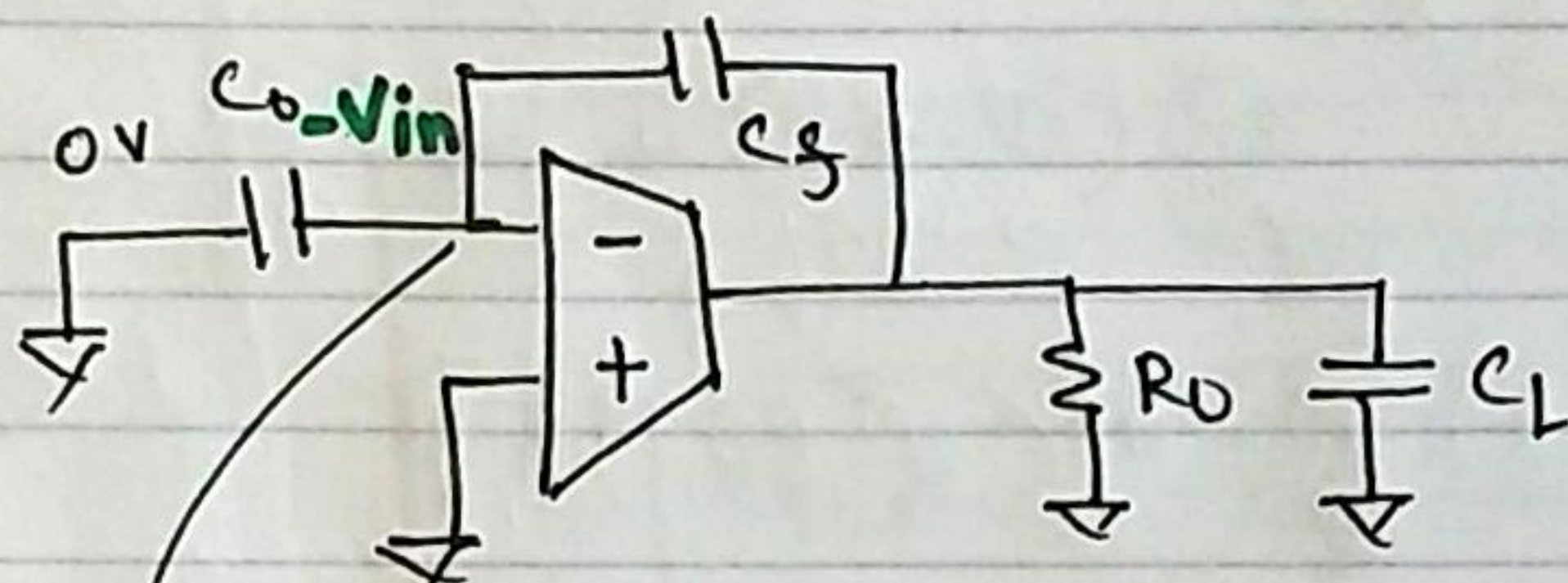


This node sees a sudden

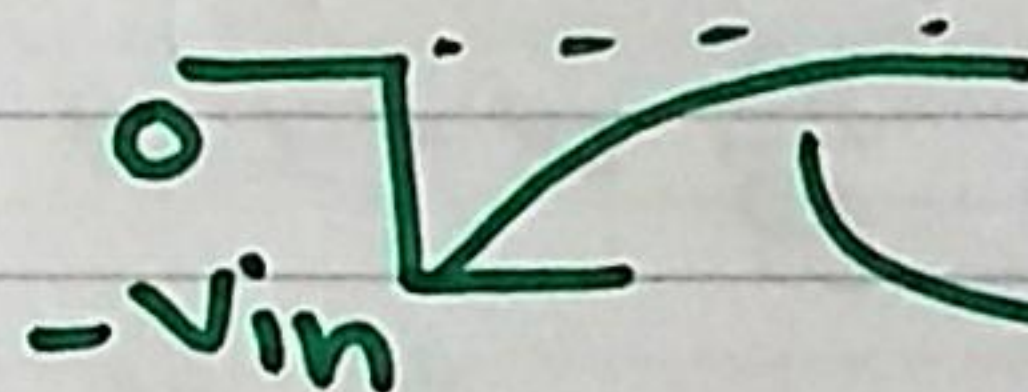voltage across a capacitor cannot change instantaneously




settling behavior


For analysis, the C_0 can be replaced by

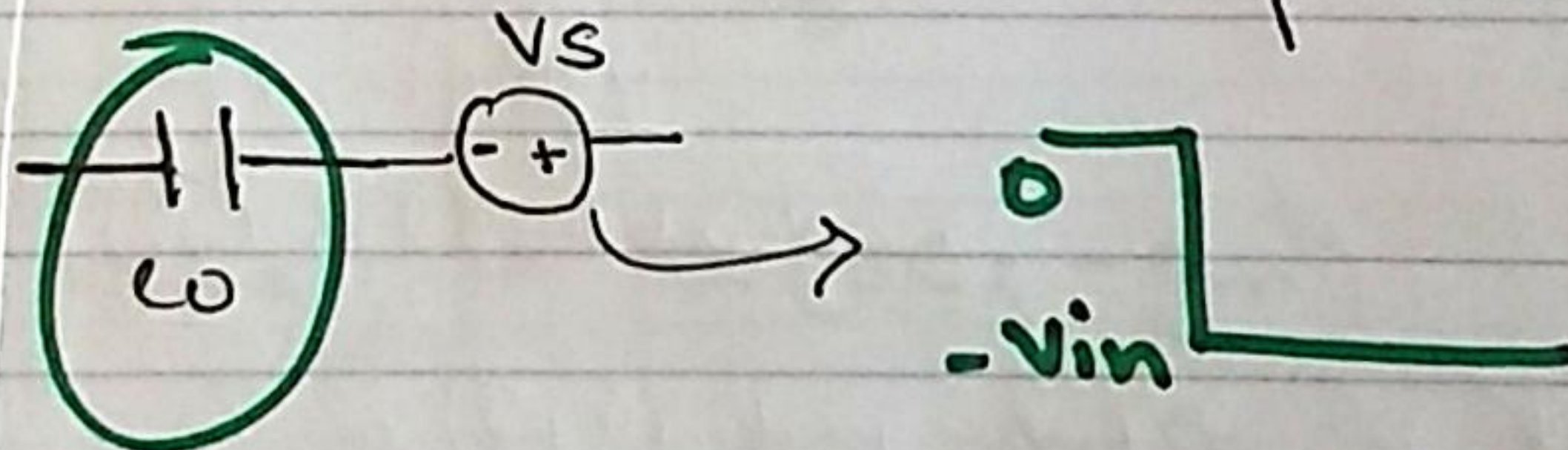

uncharged C_0

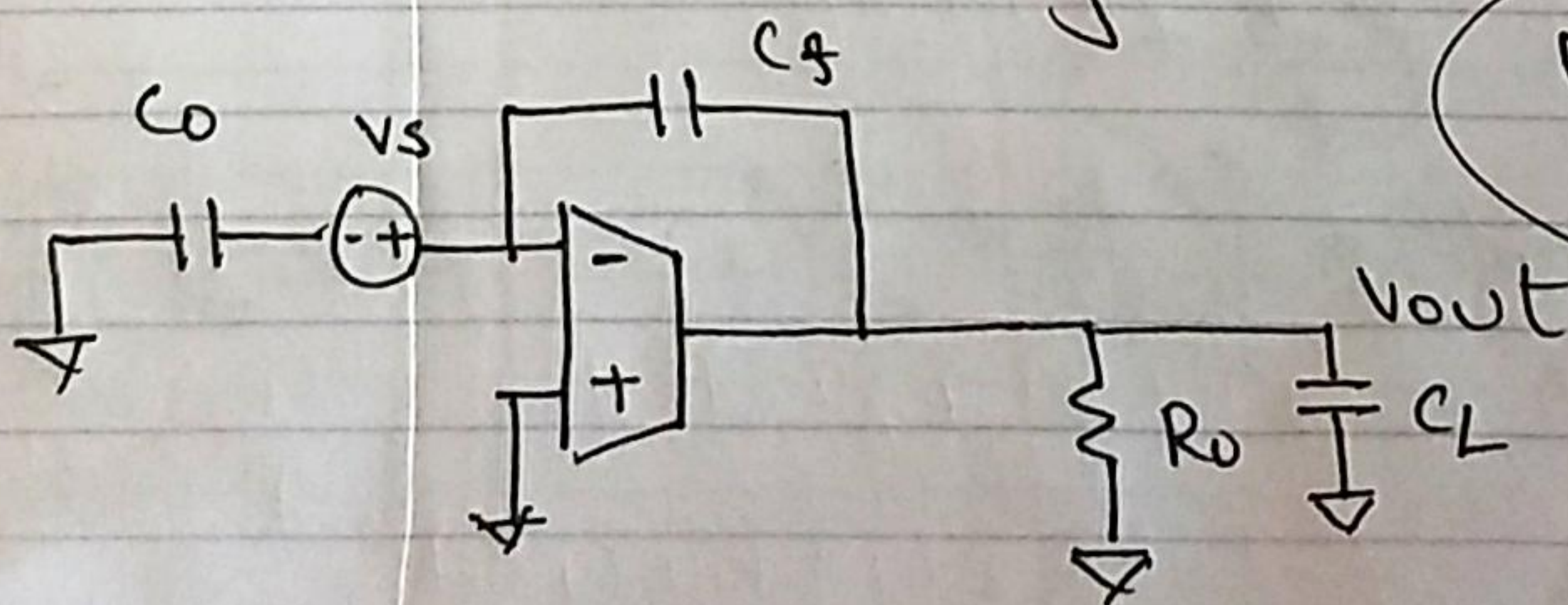

Find $\frac{V_{out}}{V_s}(s)$

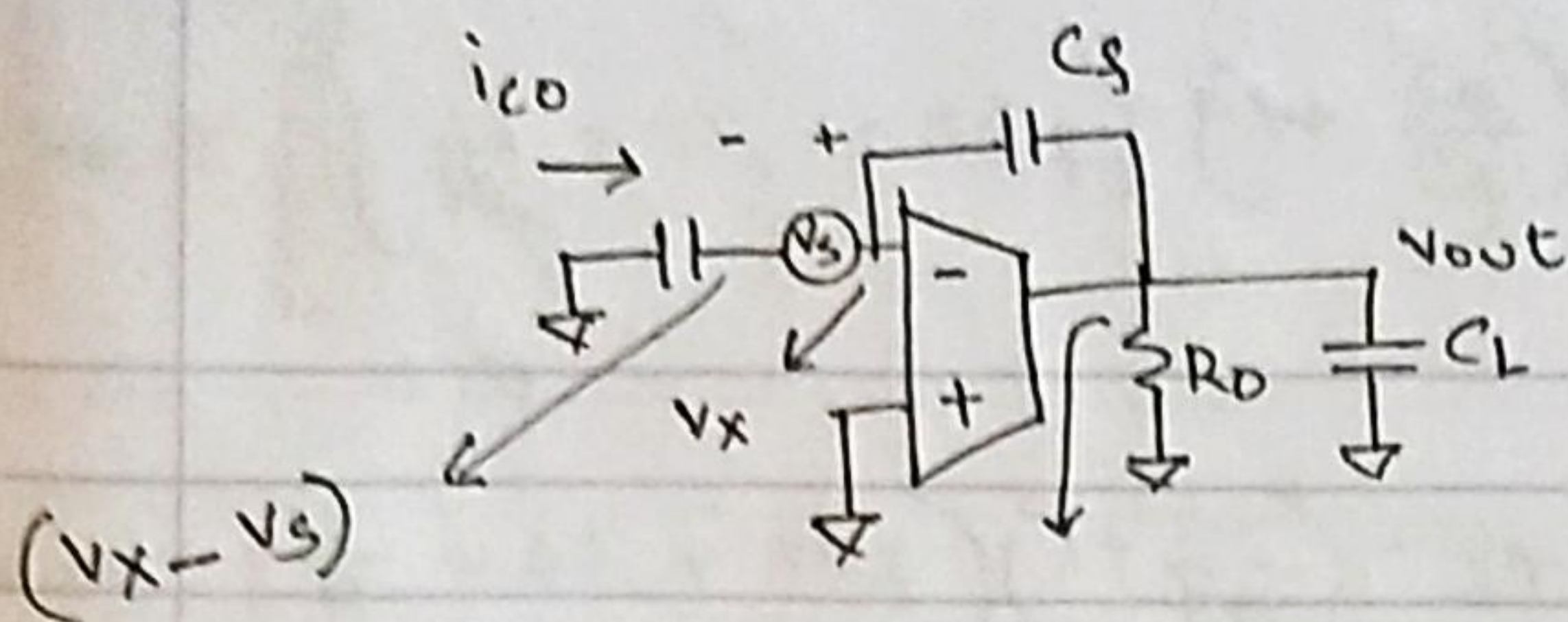

$$V_{out} \left(\frac{1}{R_D} + sC_L \right) + g_m V_x = (V_x - V_{out}) sC_f$$

$$i_{co} = - (V_x - V_s) sC_0$$

$$V_{out} = V_x - \frac{i_{co}}{sC_f}$$

$$V_{out} = V_x + (V_x - V_s) \frac{C_0}{C_f}$$

$$V_{out} = V_x \left(1 + \frac{C_0}{C_f} \right) - V_s \frac{C_0}{C_f}$$

$$\Rightarrow V_s \frac{C_0}{C_f} = V_x \left(1 + \frac{C_0}{C_f} \right) - V_{out}$$

$$\Rightarrow V_x \left(1 + \frac{C_0}{C_f} \right) = V_{out} + V_s \frac{C_0}{C_f}$$

$$\Rightarrow V_x = \frac{V_{out} + V_s \frac{C_0}{C_f}}{1 + \frac{C_0}{C_f}}$$

$$V_{out} \left(\frac{1}{R_D} + sC_L + sC_f \right) = V_x (sC_f - g_m)$$

$$= \frac{V_{out} + V_s \frac{C_0}{C_f}}{\left(1 + \frac{C_0}{C_f} \right)} (sC_f - g_m)$$

$$\Rightarrow V_{out} \left[\left(\frac{1}{R_D} + sC_L + sC_f \right) \left(1 + \frac{C_0}{C_f} \right) \right] = (V_{out} + V_s \frac{C_0}{C_f}) (sC_f - g_m)$$

$$\Rightarrow V_{out} \left[\left(\frac{1}{R_o} + sC_L + sC_f \right) \left(1 + \frac{C_o}{C_f} \right) + g_m - sC_f \right] = -g_m V_s \frac{C_o}{C_f}$$

$$\Rightarrow V_{out} \left[\left(\frac{1}{R_o} + sC_L + sC_f \right) \left(1 + \frac{C_o}{C_f} \right) + g_m - sC_f \right] = -g_m V_s \frac{C_o}{C_f}$$

$$\Rightarrow V_{out} \left[\frac{1}{R_o} \left(1 + \frac{C_o}{C_f} \right) + sC_L \left(1 + \frac{C_o}{C_f} \right) + sC_o + g_m \right] = -g_m V_s \frac{C_o}{C_f}$$

$$\Rightarrow \frac{V_{out}}{V_s} = \frac{-g_m \frac{C_o}{C_f}}{\frac{1}{R_o} \left(1 + \frac{C_o}{C_f} \right) + sC_L \left(1 + \frac{C_o}{C_f} \right) + sC_o + g_m}$$

$$= \frac{-g_m C_o}{\frac{1}{R_o} (C_o + C_f) + sC_L (C_o + C_f) + sC_o C_f + g_m}$$

$$= \frac{-g_m C_o}{\frac{1}{R_o} (C_o + C_f) + s [C_L C_o + C_L C_f + C_o C_f] + g_m}$$

$$= \frac{-g_m C_o R_o}{(C_o + C_f) + s [C_L C_o + C_L C_f + C_o C_f] + g_m R_o}$$

$$= \frac{-g_m C_o R_o}{g_m R_o C_f + C_o + C_f}$$

$$= \frac{-g_m C_o R_o}{1 + \frac{s (C_L C_o + C_L C_f + C_o C_f) R_o}{g_m R_o C_f + C_o + C_f}}$$

→ (2)